

**FACULTY OF ENGINEERING & TECHNOLOGY**  
**S.E.(EC/ECT/IEC/E&C) Year Examination-June-2015**  
**Electronics Devices & Circuits-II**  
**(Revised)**

Time: Three Hours

Maximum Marks: 80

“Please check whether you have got the right question paper.”

- i) Q. No.1 and Q. No. 6 are compulsory
- ii) Solve any two questions from remaining question in each section.
- iii) Assume suitable data wherever necessary.
- iv) Figures to right indicate full marks.

## SECTION-A

- Q.1 Solve any five of the following 10
- a) Enlist application of laser & Gunn diode.
  - b) Why heat sink is necessary in power amplifier.
  - c) Enlist features of op-amp.
  - d) How power amplifier is different than voltage amplifier.
  - e) What is pulse amplifier? What are its types?
  - f) Draw the symbol of schottky diode & Tunnel diode
  - g) Define cross over distortion in power amplifier.
  - h) Enlist application power amplifier.
- Q.2 07
- a) Explain in detail TRAPATT & BARIT diodes.
  - b) Explain class-c amplifier with characteristics. 08
- Q.3) 07
- a) Explain with neat diagram Read diode.
  - b) Explain in detail characteristic of OP-amp. 08
- Q.4 07
- a) Explain class-B complementary symmetry amplifier.
  - b) Explain AC analysis of differential amplifier 08
- Q.5 15
- Write short notes on
- a) CCD`s
  - b) Class AB amplifier
  - c) Op-amp and its features.

## SECTION-B

- Q.6 10
- Attempt any five
- a) Explain working principle of clipper.
  - b) What is symmetrical & asymmetrical triggering?
  - c) Enlist different wave shaping circuits.
  - d) Define clamper? Give two applications.
  - e) Specify coupling used in all multivibrators.
  - f) Classify non-sinusoidal oscillators.
  - g) Enlist general features of time based signal.
  - h) Why astable multivibrators are also called as free running relaxation oscillators.
- Q.7 07
- a) What are the unbiased and biased clampers. Explain in detail.
  - b) Explain in detail Schmitt trigger circuits. 08

- Q.8 a) What are positive clippers? Explain in detail. 07  
b) Explain in detail methods for controlling pulse duration for blocking oscillators. 08
- Q.9 a) A monostable multivibrator is required to convert a 100 KHz, 30% duty cycle square wave to a 100 KHz, 50% duty cycle square wave. Find the values of  $R_3$  and  $C_1$  07  
b) Explain RC controlled blocking oscillator. 08
- Q.10 Write short notes on 15  
a) Miller time based generator,  
b) Astable multivibrator.  
c) Voltage time based generator.