

FACULTY OF ENGINEERING
BE(EEE/EEP/EE) Examination - DEC – 2014
Flexible AC Transmission Systems(Revised)

[Time: THREE Hours]

[Max. Marks: 80]

“Please check whether you have got the right question paper.”

- i) Question no. 1 and 6 are compulsory.
- ii) Attempt from each section any two questions from the remaining questions.
- iii) Assume suitable data wherever necessary.

SECTION- A

- Q1 Solve any five questions: (10)
- i) What is the necessity of compensation?
 - ii) How is reactive power controlled in the electrical networks?
 - iii) What is meant by STATCOM?
 - iv) What are different types of facts controlling devices?
 - v) What is the TCSC?
 - vi) Which types of harmonics are percent in the o/p of 3 bridge convertor?
 - vii) What is the cause for voltage instability?
 - viii) What are the advantages of the slope in the SVC dynamic characteristics?
- Q2 a) Explain how power flows & types of powers in ac systems? (08)
b) What are the factors which limits loading capacity? (07)
- Q3 a) How shunt compensation is classified? Explain in detail. (08)
b) Explain the functional control scheme for FC-TCR (07)
- Q4 a) Explain the working principle and V-I characteristics of the STAT COM? (08)
b) Compare STATCOM with SVC (07)
- Q5 a) Explain the merits and demerits of hybrid compensators. (07)
b) Explain TSR & TCR by covering the following points. I) Diagram ii) operation (08)
iii)V-I characteristics.

SECTION-B

- Q6 Solve any five questions. (10)
- i) Write the application of SVC?
 - ii) Define passive and active VAR control.
 - iii) What will happen if the SVC absence in a power system network?
 - iv) What do you meant by load compensation?
 - v) List out the application of UPFC
 - vi) Define the function of control system on SSSC.
 - vii) How power flow takes place in parallel electrical system?
 - viii) How TCBR is used to improve the transient stability?
- Q7 a) Explain the hybrid phase angle regulator. (08)
b) Explain the objectives of voltage and phase angle regulation. (07)
- Q8 a) Explain the NGH-SSR damping scheme with circuit diagram. Wave form. (08)
b) Explain the basic operating control schemes for TCSC. (07)
- Q9 a) Differentiate clearly between on UPFC & IPFC (08)
b) How an UPFC scheme can be implemented using two back to back voltage source convectors. (07)
- Q10 a) Explain GTO thyristor controlled series capacitor. (08)
b) With the help of power angle curve explain how transient stability is improved of series controllers. (07)