

**FACULTY OF ENGINEERING & TECHNOLOGY**  
**M.E.(Electrical power Systems) Examination - DEC – 2014**  
**Computer Aided Power System Analysis(Revised)**

[Time: THREE Hours]


[Max. Marks: 80]

“Please check whether you have got the right question paper.”


- i) Answer any two question from section A & any two from section B
- ii) Assume suitable data, if required

SECTION- A

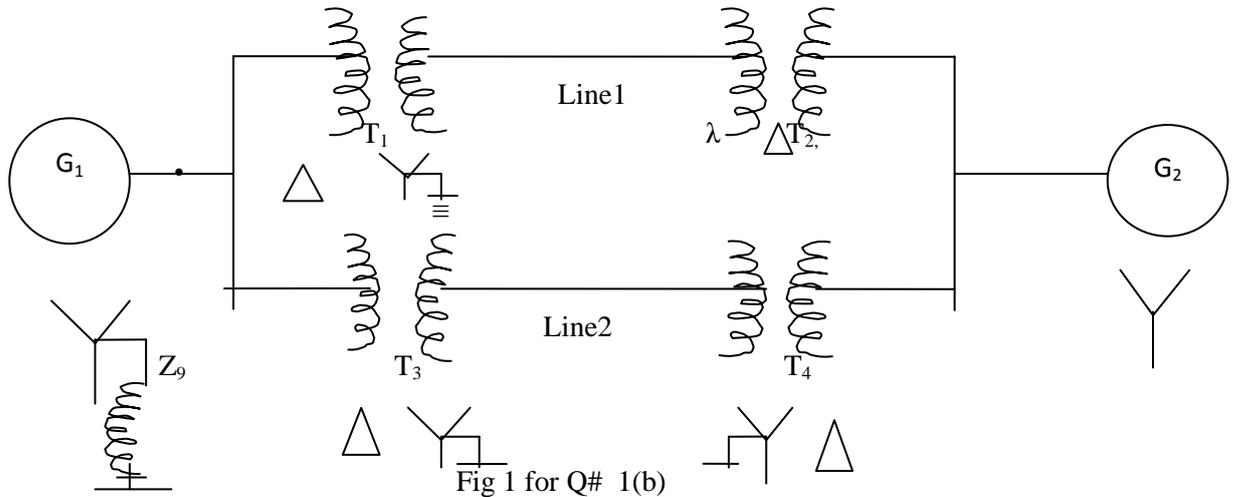- Q1 a) Explain the principle of symmetrical components. What is the difference between positive and negative sequence components? Derive the relation between  $V_a, V_b, V_c$  and  $V_{a_0}, V_{a_1}$  and  $V_{a_2}$ . And also given  $V_{a_0}, V_{a_1}, V_{a_2}$  derive the equation to obtain  $V_a, V_b, V_c$  (10)
- b) Draw the positive negative and zero sequence networks of the power system as shown in fig 1 (10)



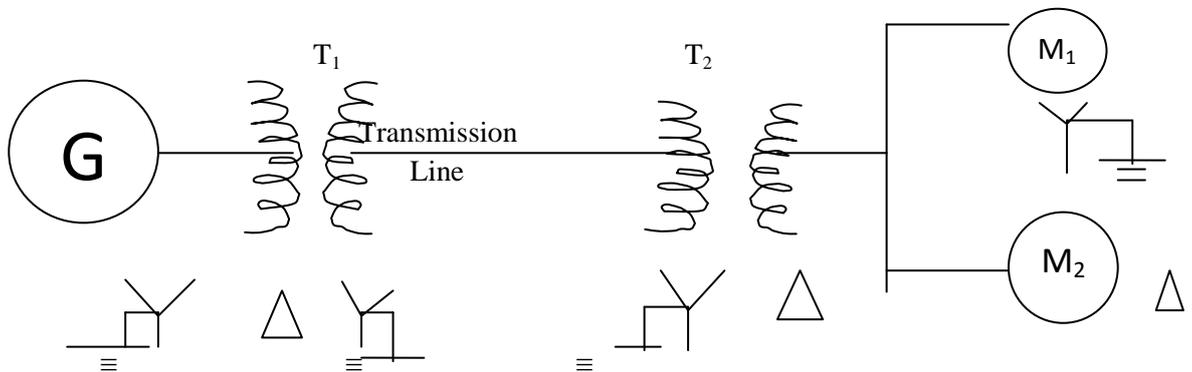
- Q2 a) Explain the significance of per unit system in power system analysis & list the advantages of P.U. system. (08)
- b) a 90 MVA, 11 KV, 3 phase generator has a reactance of 25%. The generator supplies two motor through transformers and transmission line as shown in fig. 2. The transformer  $T_1$  is a 3-phase transformer, 100 MVA, 10,132 KV, 6% reactance. The transformer  $T_2$  is composed of 3-single phase units each rated at 30 MVA, 66 KV/10 KV with 5% reactance. The connections of  $T_1$  and  $T_2$  are as shown. The motors are rated at 50 MVA and 40 MVA both 10 KV and 20% reactance. Taking the generator rating as base, draw reactance diagram and indicate the reactance's in per unit. The reactance of transmission line is 100 ohms. (12)



- Q3 a) Derive the expression for faultcurrent for double line to ground fault, also draw the interconnections of sequence networks. (10)
- b) Explain the sequence impedance of a three phase synchronous generator (10)

SECTION-B

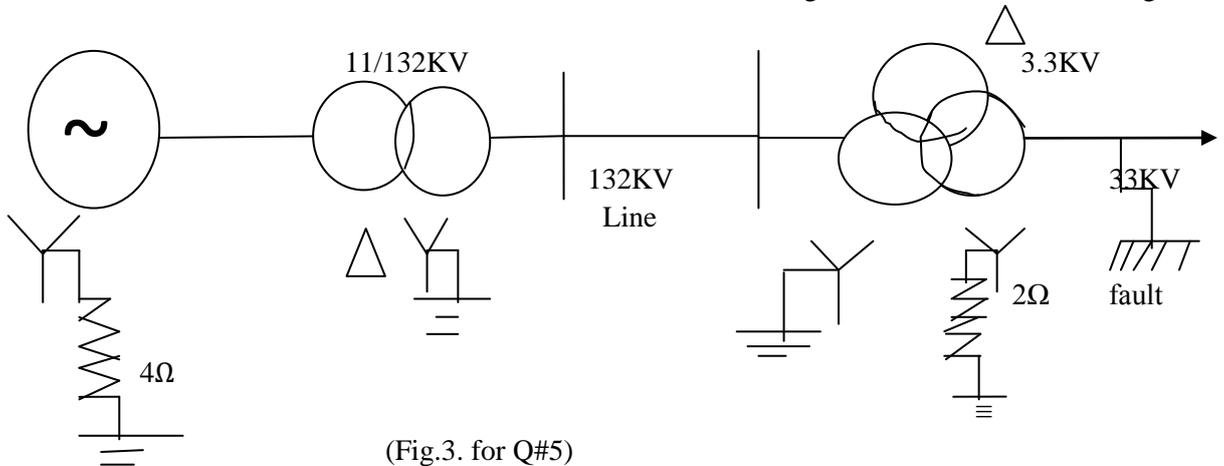- Q4 a) Explain the features concerning the formation of constraint matrix K. (10)  
 b) Explain the transformation of shunt-faults with respect to the case of single line to ground fault (10)
- Q5 A 50 MVA generator, 11 KV, 3-phases is feeding an 11/132KV, 50MVA transformer. The transformer feeds 132 KV line at the far end of which is a 132/33/3.3KV, 3 winding transformer, as shown in fig 3. (20)



The data for power system in fig. 3 is as given below.

Generator: 50 MVA, 11 KV,  $x_1=0.4$  pu.  $x_2=0.3$  pu  $x_0=0.1$  p.u. Y-connected, star-point earthed though  $4\Omega$  resistance.

two winding transformer: 50 MVA, 11KV/132 KV,  $\Delta/Y$ , star point solidly earthed,  $x_1=x_2=x_0=0.08$  p. u.

Line: 132 KV,  $x_1=x_2=20\ \Omega$  and  $x_0=50\Omega$ .

Three winding transformer: 50 MVA, 132/33/3.3KV, 132 KV winding solidly earthed, 33 KV winding earthed through  $2\ \text{ohm}$  resistance, 3.3 KV winding  $\Delta$ -connected. 132KV winding,  $x_1=x_2=x_0=0.05$  p.u., 33KV winding,  $x_1=x_2=x_0=0.04$  p.u, 3.3 KV winding,  $x_1=x_2=x_0=0.06$  p. u. A single line to ground fault occurs on one of the phases at 33 KV terminals. Find the fault-current and fault MVA.

- Q6 a) State the advantages & disadvantages of Gauss-seidel method & Newton -Raphson method for power flow (10) solution.  
 b) With neat flow chart explain the power flow solution of Gauss. Seidel method. (10)